

1. (12 points) The circuit is shown in Figure 1.

(1) Use mesh analysis to obtain u_1 .

(2) Calculate the power absorbed by the voltage source.

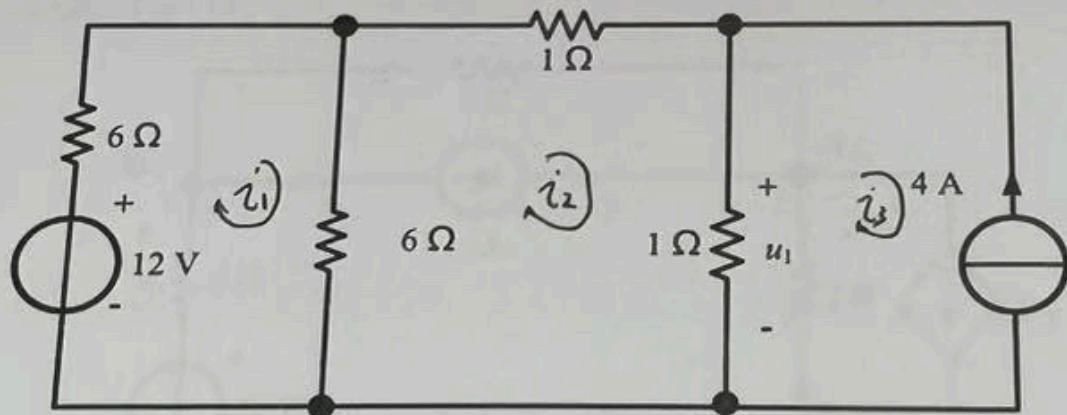


Figure 1

2. (14 points) The circuit is shown in Figure 2.

(1) Use superposition to obtain i_1 .

(2) Employ node analysis to determine i_1 and compare the outcome with that obtained in (1).

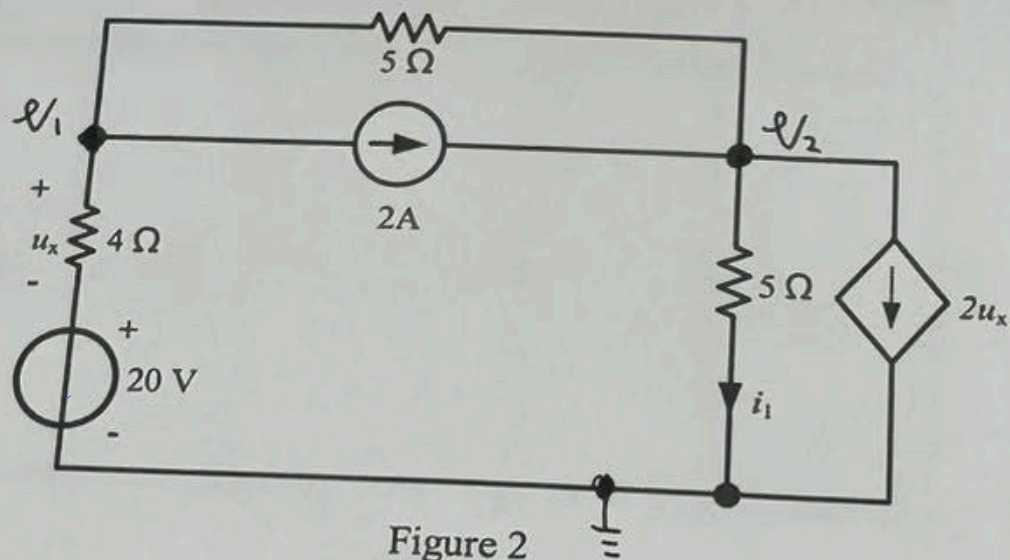


Figure 2

5.0

3. (16 points) The circuit is shown in Figure 3.

- (1) Determine the Thevenin equivalent with respect to terminals a and b for the circuit, excluding the variable resistor R_x .
- (2) Obtain the maximum power consumed by the variable resistor R_x .

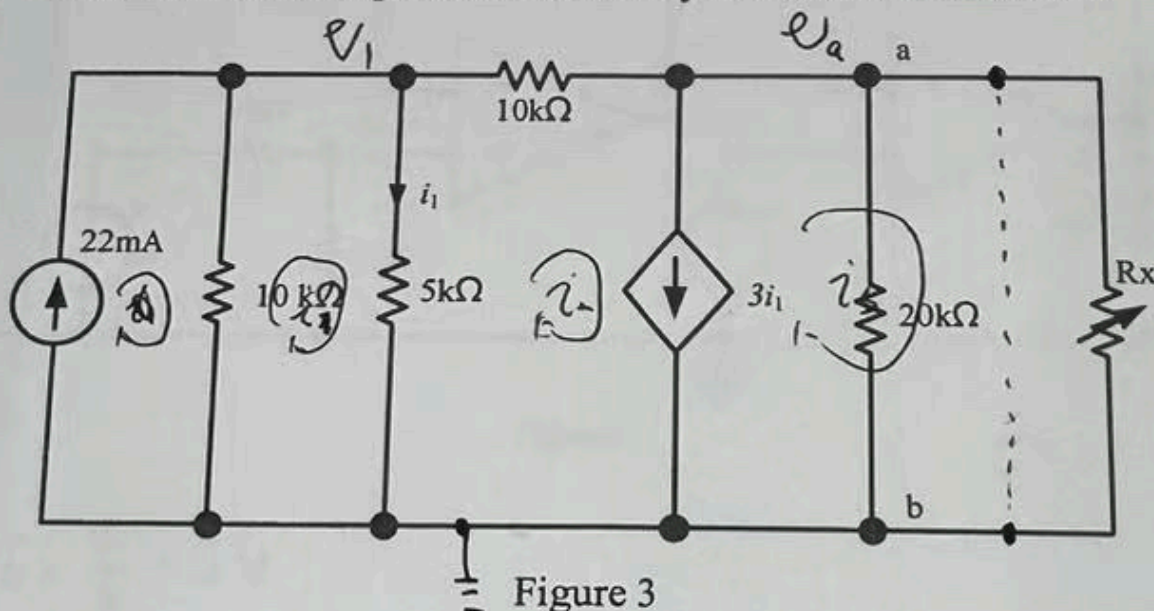


Figure 3

4. (12 points) The operational amplifiers in the circuit are ideal and operate in their linear range. Obtain u_o in the circuit.

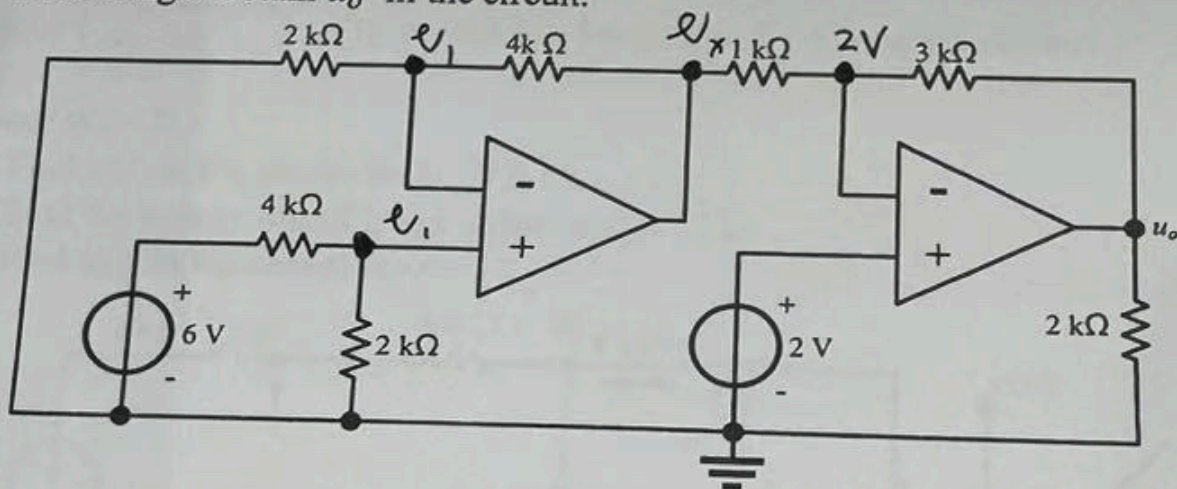



Figure 4

5. (16 points) The circuit is shown in Figure 5. The voltage source $v_S(t)$ satisfies

$$v_S(t) = \begin{cases} 1 \text{ V}, & 0 \leq t \leq 1 \text{ s} \\ t \text{ V}, & t > 1 \text{ s} \end{cases}$$

closed at $t = 0$.

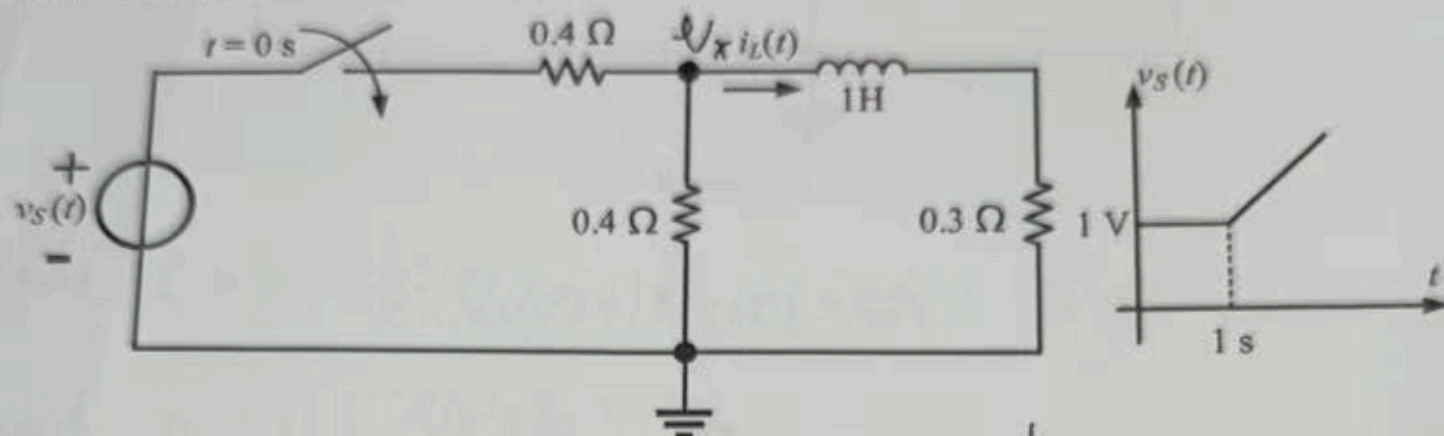- (1) Find $i_L(t)$ in the circuit for $0 \leq t \leq 1 \text{ s}$.
- (2) Find the energy stored in the inductor at $t = 1 \text{ s}$.
- (3) Find $i_L(t)$ in the circuit for $t > 1 \text{ s}$.



6. (14 points) The circuit is shown in Figure 6. At $t = 0^-$, $v_C(0^-) = 0 \text{ V}$ and $i_L(0^-) = 0 \text{ A}$. Find $v_C(t)$ in the circuit ($t > 0$).

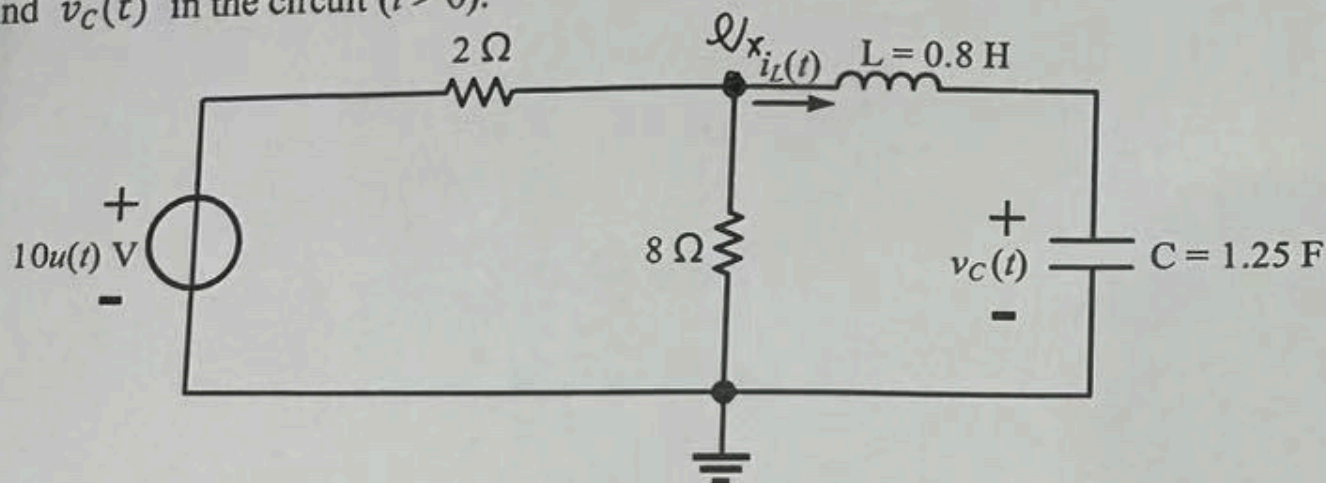


Figure 6

16 7. (16 points) The circuit is shown in Figure 7. $v_S(t) = e^{-0.5t}$ V. At $t = 0^-$, $v_{C1}(0^-) = 0$ V and $v_{C2}(0^-) = 0$ V. Find $v_{C2}(t)$ in the circuit ($t > 0$).

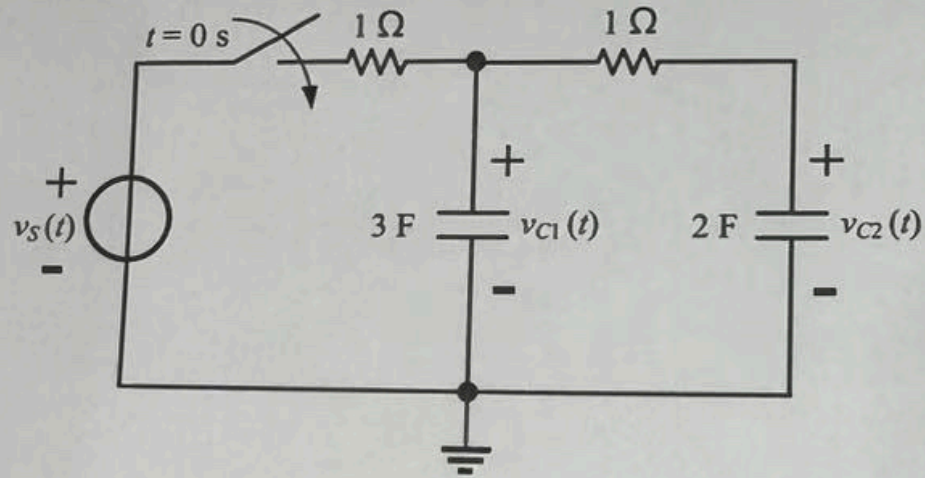


Figure 7